



University of Bahrain

CE -- CIT -- UOB


# TEST 1 (9 Nov 2015) ITCE363: Electronics 2

Dr. Riyadh Al-Hakim

## Q1. [60 marks]

In the following amplifier, the OP AMPs are 741 in which  $f_T = 1$  MHz and slew rate =  $0.5$  V/ $\mu$ s.

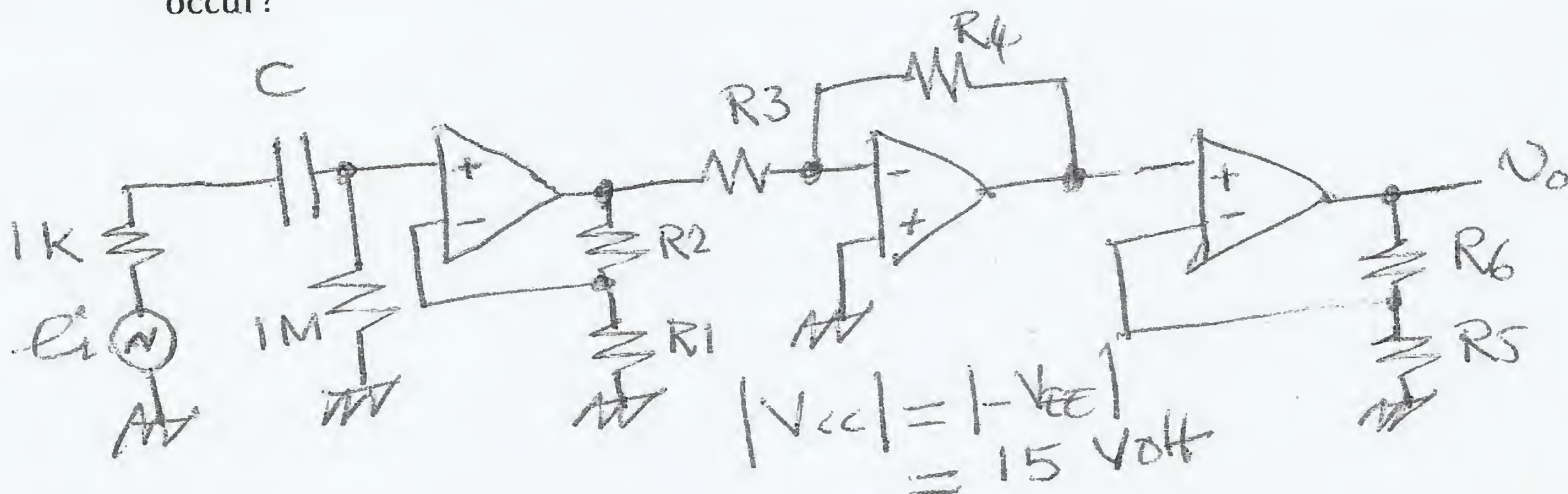1. Find  $R_1, R_2, R_3, R_4, R_5$  and  $R_6$  that make the mid-band gain value of each stage = 5
2. Find  $C$  that makes  $f_{low}$  cutoff freq. = 100 Hz
3. Calculate the small signal bandwidth.
4. Calculate the gain in dB at  $f = 10$  Hz, 25 Hz, 1 kHz, 100 kHz and 250 kHz.
5. What maximum input signal amplitude can you use before **clipping** distortion starts to occur?
6. What maximum input signal frequency can you use before **slew rate** distortion starts to occur?



## Q2. [40 marks]

In the following amplifier, assume  $R_1 = R_2 = 120$  k $\Omega$ ,  $C_{c1} = C_{c2} = C_E = \infty$ ,  $L_T = 25$   $\mu$ H with  $2$   $\Omega$  internal resistance,  $r_{out}$  of the transistor =  $50$  k $\Omega$ , assume  $C_{stray}$  of o/p =  $10$  pF:

- a) Find  $R_E$  for  $I_C = 0.5$  mA. Find  $V_{CE}$ . Assume  $V_{CC} = 12$  volt.
- b) Find  $C_T$  that tunes the amplifier at  $1.5$  MHz
- c) Find  $f_1, f_2$  and the BW of the amplifier
- d) Find the voltage gain in dB at resonance and at  $f_1$  and  $f_2$ .
- e) If this amplifier is driving  $R_L = 10$  k $\Omega$ , what will be the new BW and voltage gain.

